

(CSIT) Student at Madan Bhandari Memorial College

2073

Full Marks: 60

Pass Mark: 32

Time: 3 hours

The figures in the margin indicate full marks.

Attempt any two questions:

(10x2=20)

- Attempt any eight questions.**

(8x5=40)

4. Convert the following hexadecimal number to decimal and octal numbers.
a) 4FFF b) 6FED
5. Explain the error code detection code with example.
6. Explain the duality theorem with example.
7. Design a half adder logic circuit using only universal gates.
8. Draw a logic circuit of 8 x 1 multiplexer.
9. Design the 4 bit parallel Binary adder.
10. Explain the PCA with block diagram.

11. Explain the R-S flip – flop with truth table.
12. Explain the shift register with example.
13. Write short notes on (**any two**):
 - a) Binary counter
 - b) State Reduction
 - c) Negative edge triggering